

PRASTUTI'26



AUTOMATED VENDING MACHINE CONTROLLER

Modern campuses rely heavily on automated systems to improve efficiency and reduce human intervention. One such system is the **Automated Vending Machine**, which allows users to purchase products quickly using digital payment or coin-based mechanisms.

Your task is to design a **digital controller for a vending machine** that accepts coins, processes product selection, and dispenses the selected item.

The controller must ensure correct transaction handling, maintain system states, and manage product dispensing using digital logic circuits.

System Description

The vending machine offers three products:

Product	Price
Product A	₹10
Product B	₹15
Product C	₹20

Users insert coins and select a product.

The vending machine must verify whether the **inserted amount is sufficient** and then dispense the selected item.

If the inserted amount is greater than the product price, the system must **return the remaining balance as change**.

Inputs

1. ₹10 Coin Input
2. ₹20 Coin Input
3. **Product Selection Buttons**

- Product A
- Product B
- Product C

4. Reset Signal

Outputs

1. Product Dispense Signals

- Dispense A
- Dispense B
- Dispense C

2. Change Return Indicator and amount returned

3. Insufficient Balance Indicator

Tasks

1 Coin Detection and Encoding

Design a system that detects inserted coins and encodes them into digital signals.

Points: 25

2 Transaction Controller

Design a **Finite State Machine (FSM)** that manages vending machine operations.

Possible states include:

- Idle
- Coin Insert
- Product Selection
- Product Dispense
- Change Return

Participants must provide:

- State diagram
- State transition table
- Logic implementation

Points: 40

3 Product Selection Logic

Implement a system that compares the **inserted balance with product price** and determines whether the product can be dispensed.

Points: 20

4 Output Control System

Generate appropriate output signals for:

- Product dispensing
- Change return
- Insufficient balance indication

Points: 15

Implementation Rules

The circuit must be implemented **only using digital logic components**, such as:

- Logic Gates
- Flip-Flops
- Counters
- Encoders / Decoders
- Multiplexers / Demultiplexers
- Comparators

✗ Microcontrollers are **not allowed**.

The entire system must be designed and simulated using **Proteus Design Suite**.

★ Bonus Challenge (Extra 20 Points)

Verilog HDL Implementation

Participants may additionally implement the **Vending Machine Controller** using **Verilog HDL**.

The Verilog design should include:

- FSM-based transaction control
- Coin input detection
- Balance counter
- Product selection logic
- Product dispense and change return logic

Participants must submit:

- 1 Verilog module(s) implementing the system
- 2 A **testbench** verifying system functionality
- 3 Simulation waveform results

Bonus Evaluation Criteria

Component	Points
Correct Verilog implementation	10
Testbench & simulation results	5
Code structure and modularity	5

Total Bonus Points: **20**

Good luck and happy designing!